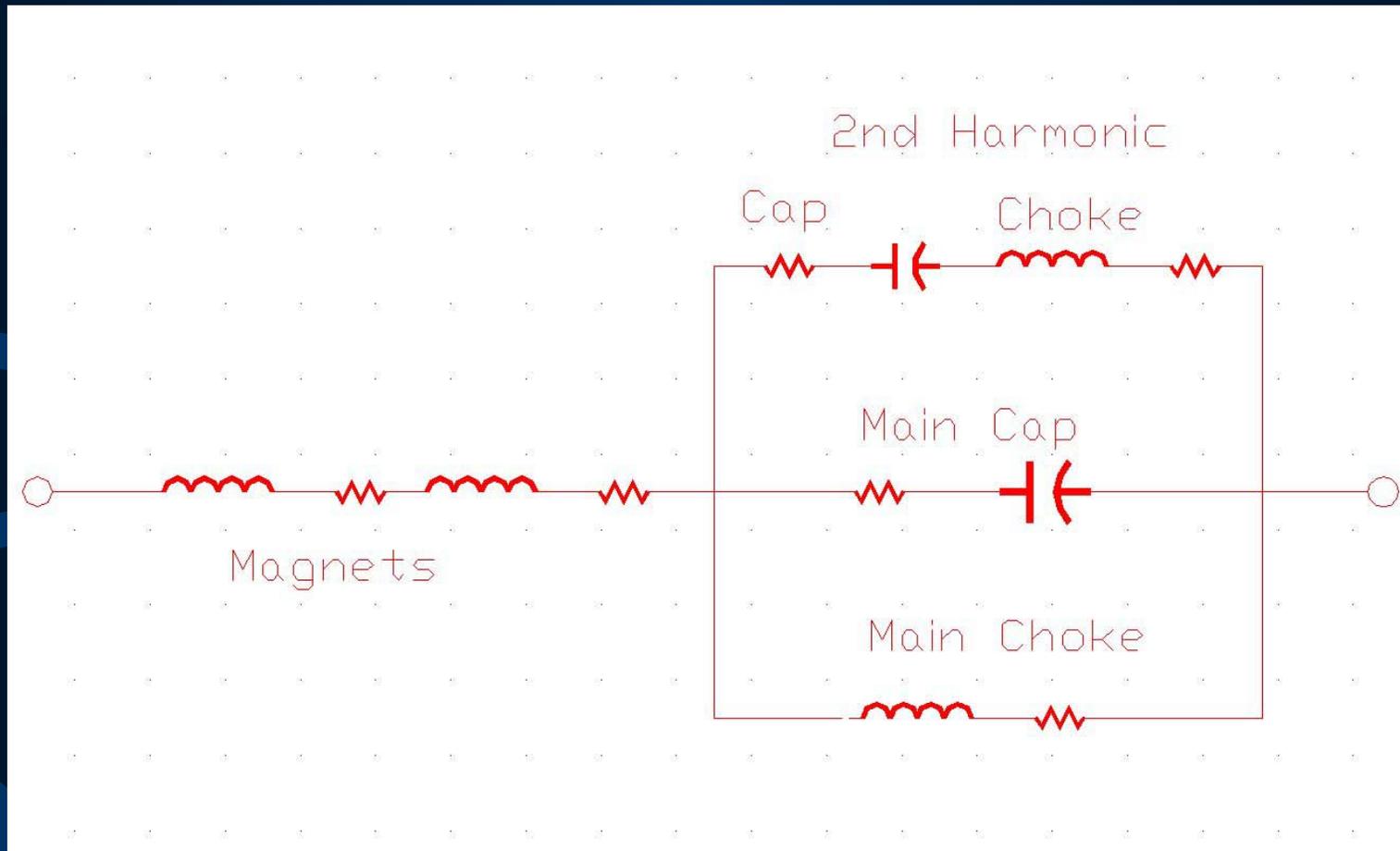


BOOSTER DUAL RESONANCE

- First look at a possible solution for a dual resonant modification to the existing Booster.
- The purpose is to decrease the maximum di/dt in booster magnets and thus free up additional RF capability.
- Goal is to keep present magnets, chokes, and capacitors.
- Add additional components as necessary

Booster Cell With 2nd Harmonic



Mathcad program for calculating component values:

Calculations For A Dual Resonant Booster

DAW 4/5/03

Impedance - neglecting losses:

$$z := \omega \cdot L_m \cdot j + \frac{1}{\left[\frac{1}{\frac{1}{\omega \cdot C_j} + \frac{1}{\omega \cdot L_{ch} \cdot j} + \left(\frac{1}{\omega \cdot L_s \cdot j + \frac{1}{\omega \cdot C_s \cdot j}} \right)} \right]}$$

First some definitions:

The two resonant frequencies desired (Hz): $f_{res1} := 15$ $f_{res2} := 30$

$$w_{res1} := 2 \cdot \pi \cdot f_{res1} \quad w_{res2} := 2 \cdot \pi \cdot f_{res2} \quad w_{sum} := (w_{res1})^2 + (w_{res2})^2 \quad w_{diff} := (w_{res2})^2 - (w_{res1})^2$$

The magnet inductance (H): $L_m := 0.0204$

The main capacitor bank (F): $C := 0.00611$

Let σ be equal to the ratio of the choke to magnet inductance: $\sigma := 1.96$ $L_{ch} := \sigma \cdot L_m$

The Main Choke Inductance: $L_{ch} = 0.04$

Let ν be equal to the ratio of the res. choke to magnet inductance: $\nu := 1.275$ $L_{res} := \nu \cdot L_m$ +

2nd Harmonic Choke Inductance: $L_{res} = 0.026$


From the analysis below η , the ratio of 2nd harmonic cap bank to main cap bank should be:

$$\eta := \frac{4 \cdot (\sigma + 1)}{(w_{sum}^2 - w_{diff}^2) \cdot (L_m \cdot C)^2 \cdot \nu \cdot \sigma} \quad \eta = 0.242 \quad C_{res} := \eta \cdot C$$

2nd Harmonic Cap Bank: $C_{res} = 1.476 \times 10^{-3}$

1st Resonance: $f_1 = 14.988$ 2nd Resonance: $f_2 = 30.025$

ATP Computer Model

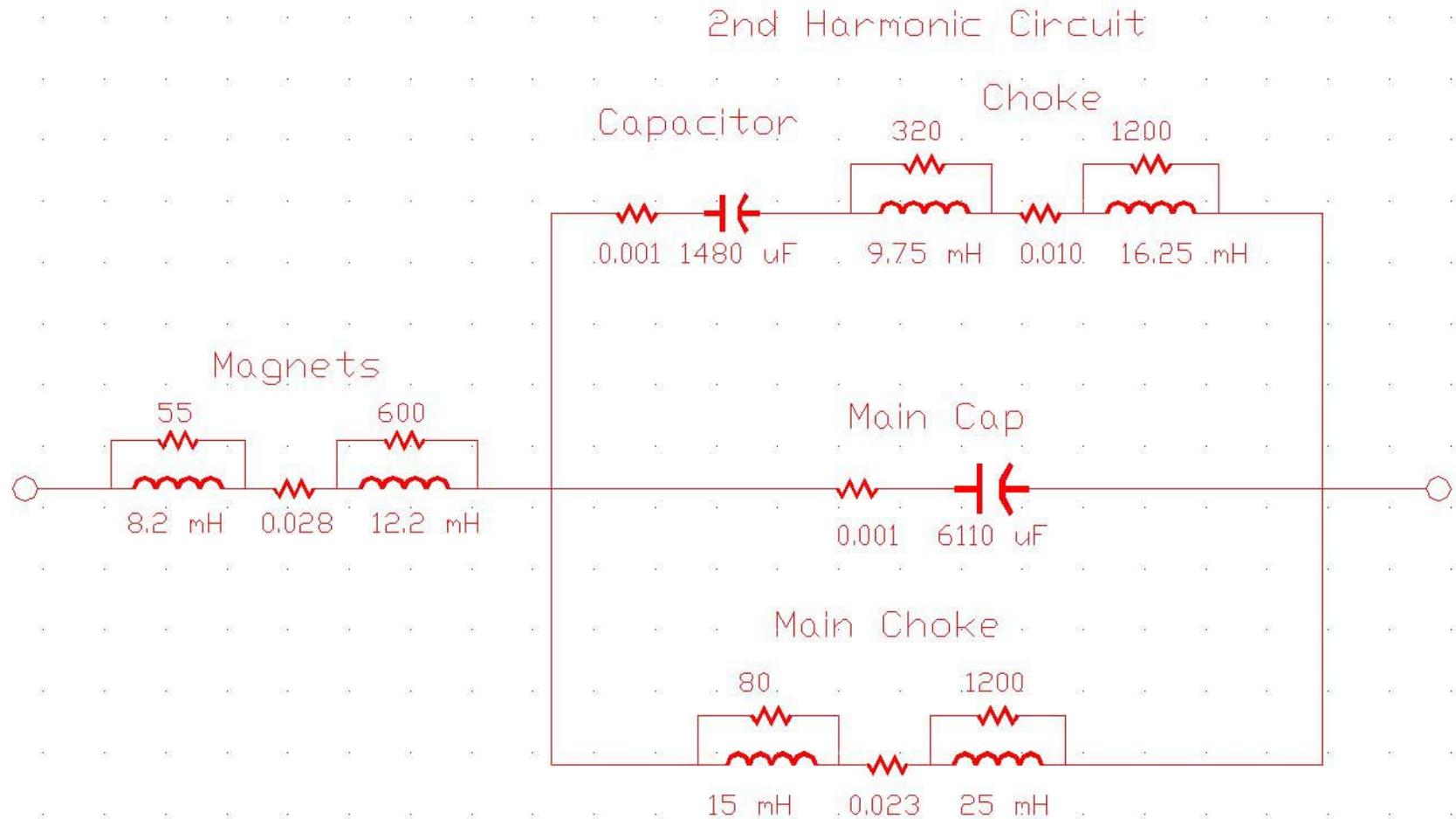

Mathcad program for investigating component sensitivity:

ADMITTANCE PLOT OF DUAL RESONANT BOOSTER daw 7/29/03

THE MAGNET: $R_{mag1} := 55.0$ $R_{mag} := 0.0028$ $R_{mag2} := 500.0$
 $L_{mag1} := 0.0082$ $L_{mag2} := 0.0122$


THE MAIN CHOKE: $R_{mck1} := 80.0$ $R_{mck} := 0.0023$ $R_{mck2} := 1200.0$
 $L_{mck1} := 0.015$ $L_{mck2} := 0.025$

THE 2ND HARMONIC CHOKE: $R_{mhm1} := 320.0$ $R_{mhm} := 0.010$ $R_{mhm2} := 1200.0$
 $L_{mhm1} := 0.00975$ $L_{mhm2} := 0.01625$


THE MAIN CAP BANK: $C_{mcap} := 0.00611$ $R_{mcap} := 0.001$

THE 2nd HARMONIC CAP BANK: $C_{mhm} := 0.001480$ $R_{hcap} := 0.001$

First Resonance:

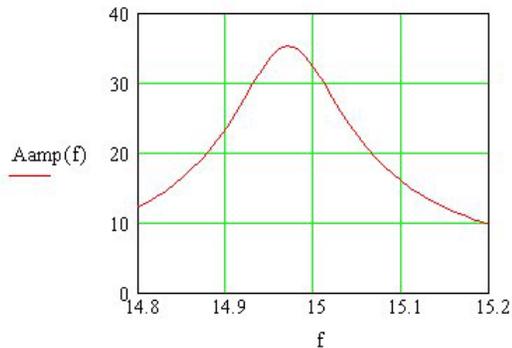

Second Harmonic:

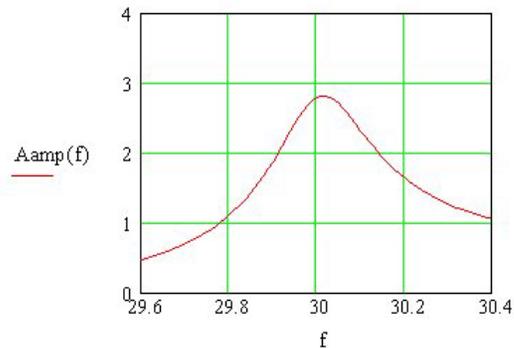

Mathcad program for calculating the 15 Hz amplitude given required peak current and the relative amplitude of the 2nd harmonic

The following analysis relates to a DUAL RESONANT booster

The purpose is to calculate the required amplitude of the first resonance given the peak current and the relative amplitude of the second resonance.

The current has the form of:

$$I_{mag} := A \cdot \cos(\theta) + B \cdot \sin(2 \cdot \theta)$$

The required peak current is: $I_{ampk} := 435.0$

The relative amplitude of the second resonance is (B/A): $\alpha := .125$


$$A := \frac{I_{ampk}}{(\cos(\theta) + \alpha \cdot \sin(2 \cdot \theta))}$$

$$A = 422.705$$

And since $B := \alpha \cdot A$


$$B = 52.838$$

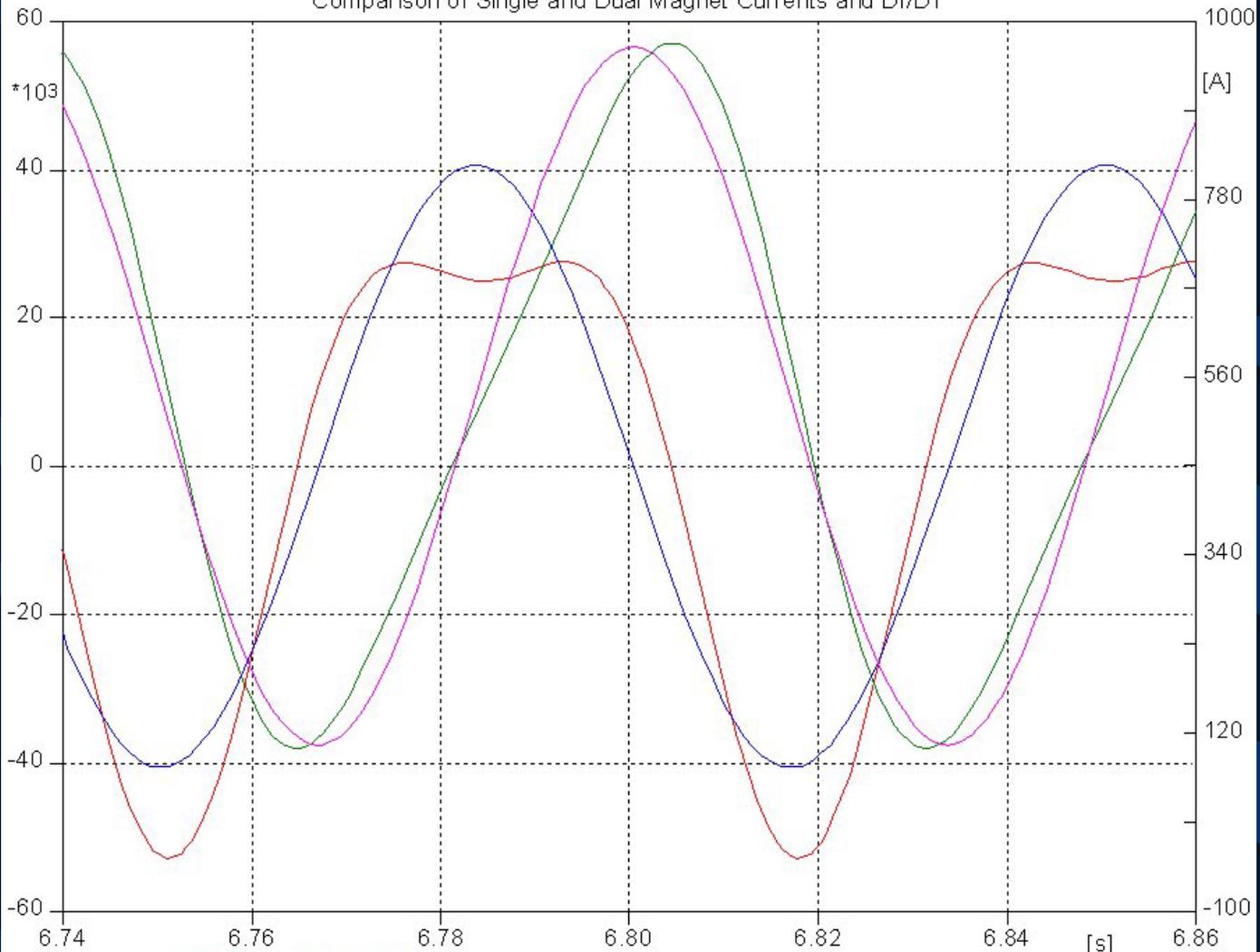BOOSTER DUAL RESONANT Comparison of Single and Dual Magnet Currents and DI/DT




dual_res.dat.pl4: t: DIDT c: VDRIV-CCR
present.dat.pl4: t: DIDT c: VDRIV-C1A

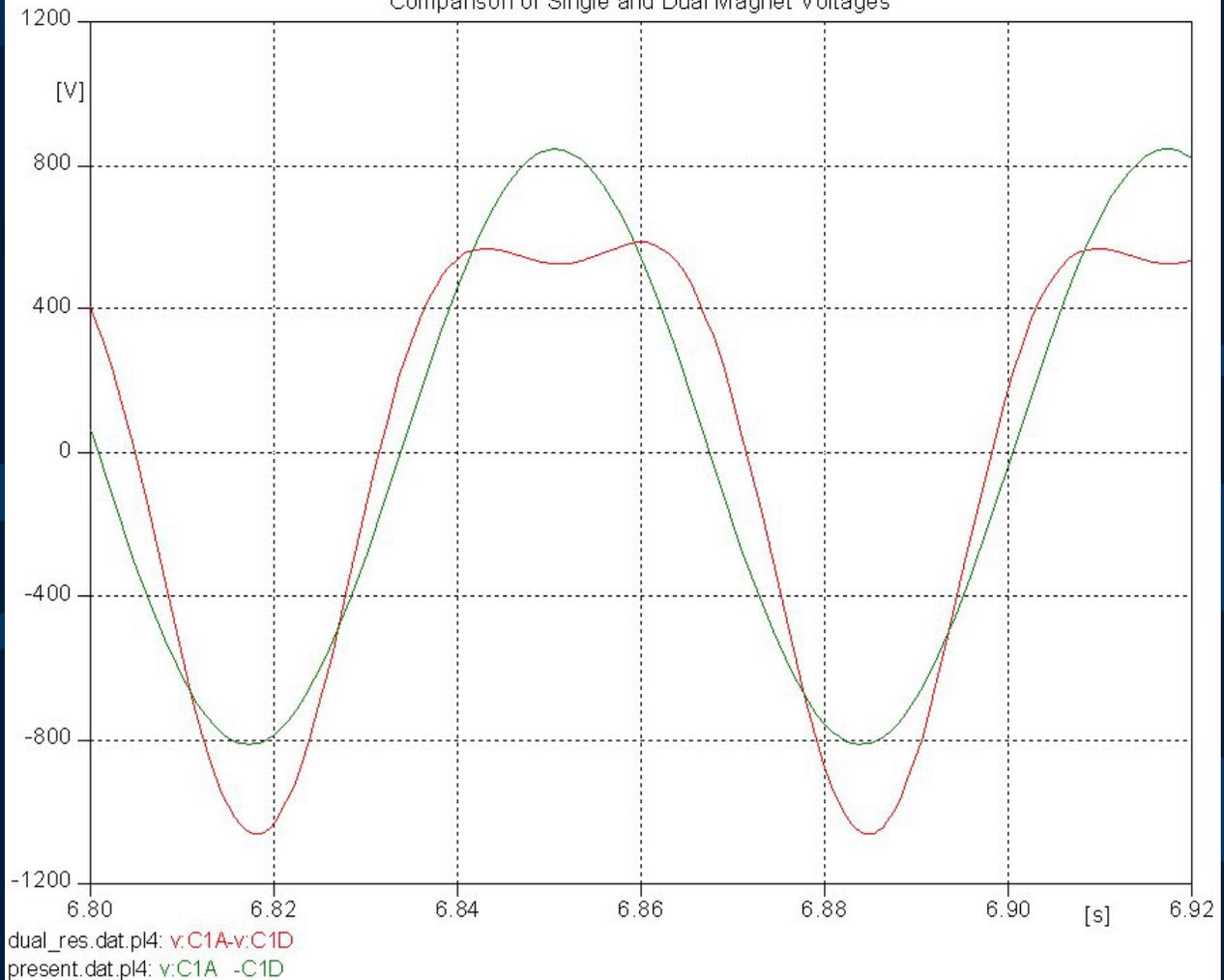BOOSTER DUAL RESONANT Comparison of Single and Dual Magnet Voltages




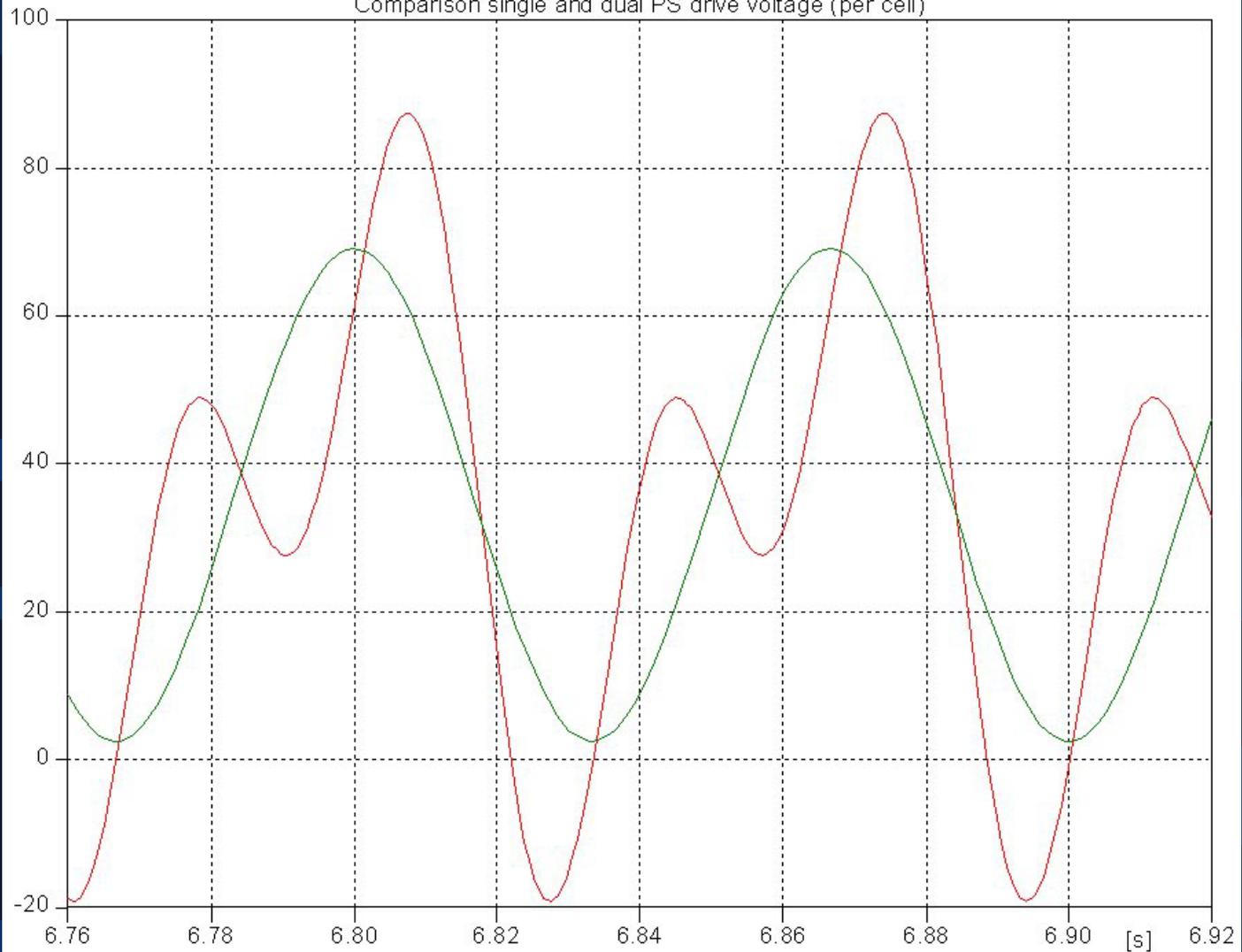BOOSTER DUAL RESONANT
Comparison single and dual PS drive voltage (per cell)



dual res.dat.pl4: t:VDRIV
factors: 0.25
offsets: 0
present.dat.pl4: v:VDRIV-VRET

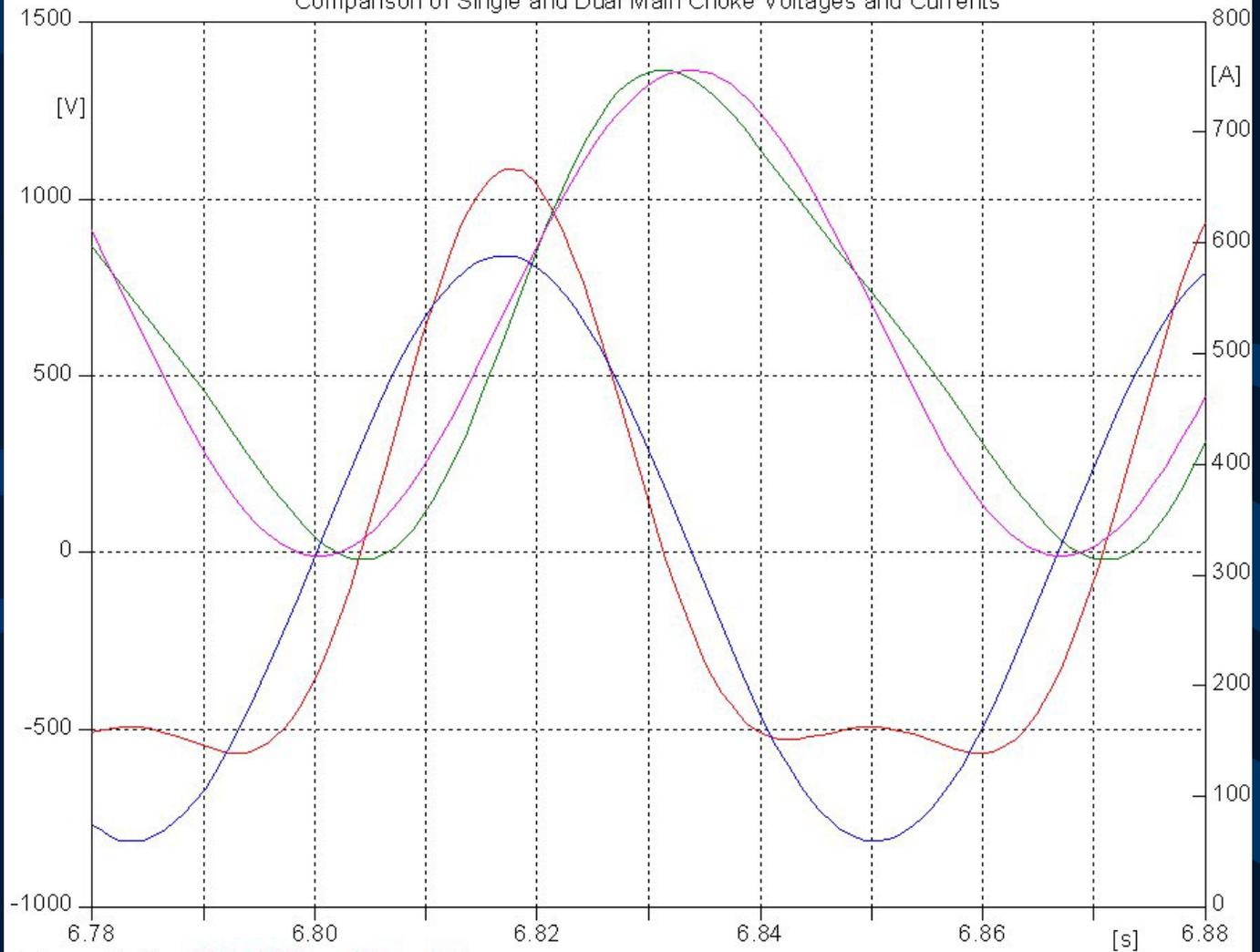
BOOSTER DUAL RESONANT
Comparison of Single and Dual Main Choke Voltages and Currents




dual_res.dat.pl4: v:C1D -C1G c:C1D -C1E
present.dat.pl4: v:C1D -C1H c:C1E -C1F

BOOSTER DUAL RESONANT

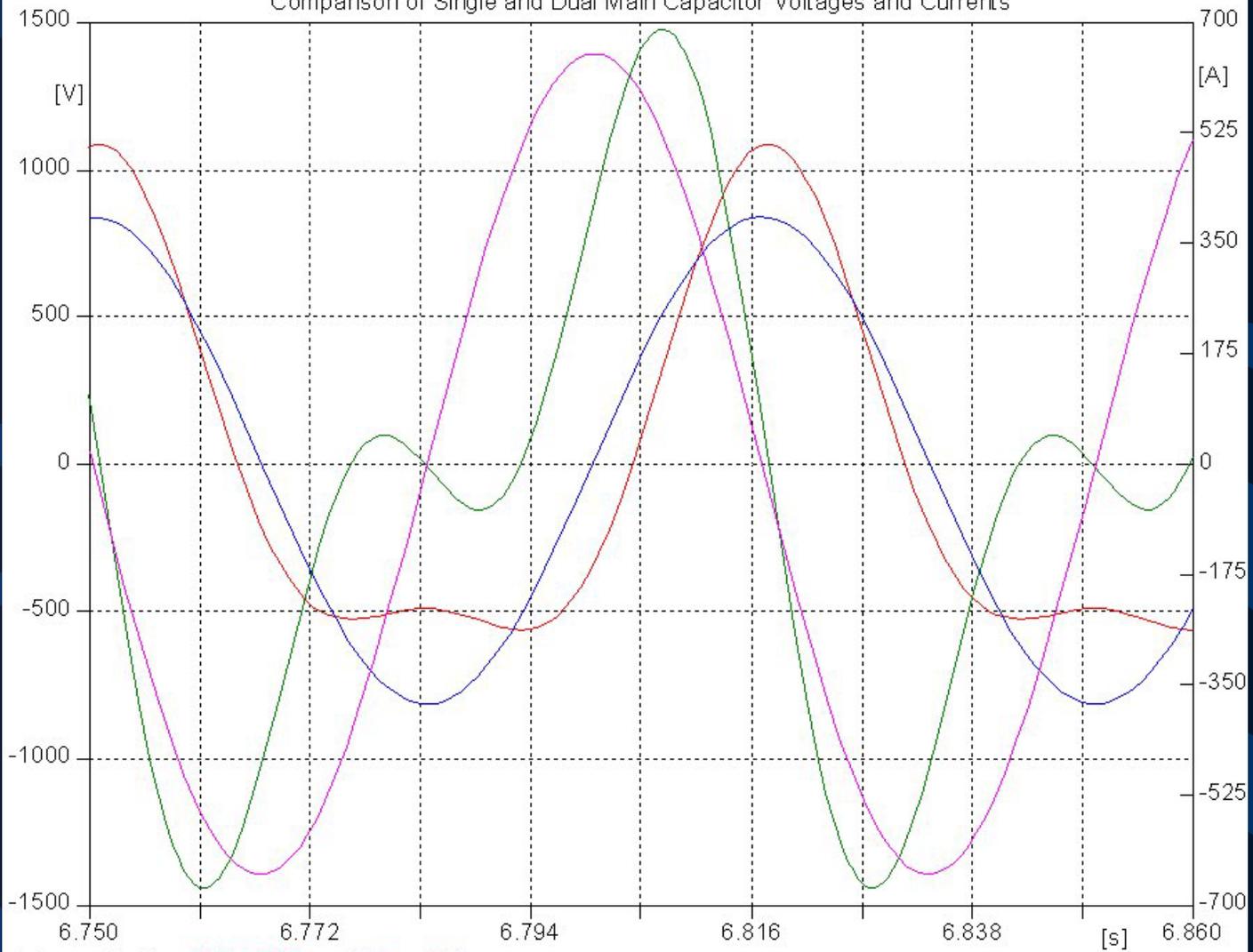Comparison of Single and Dual Main Capacitor Voltages and Currents



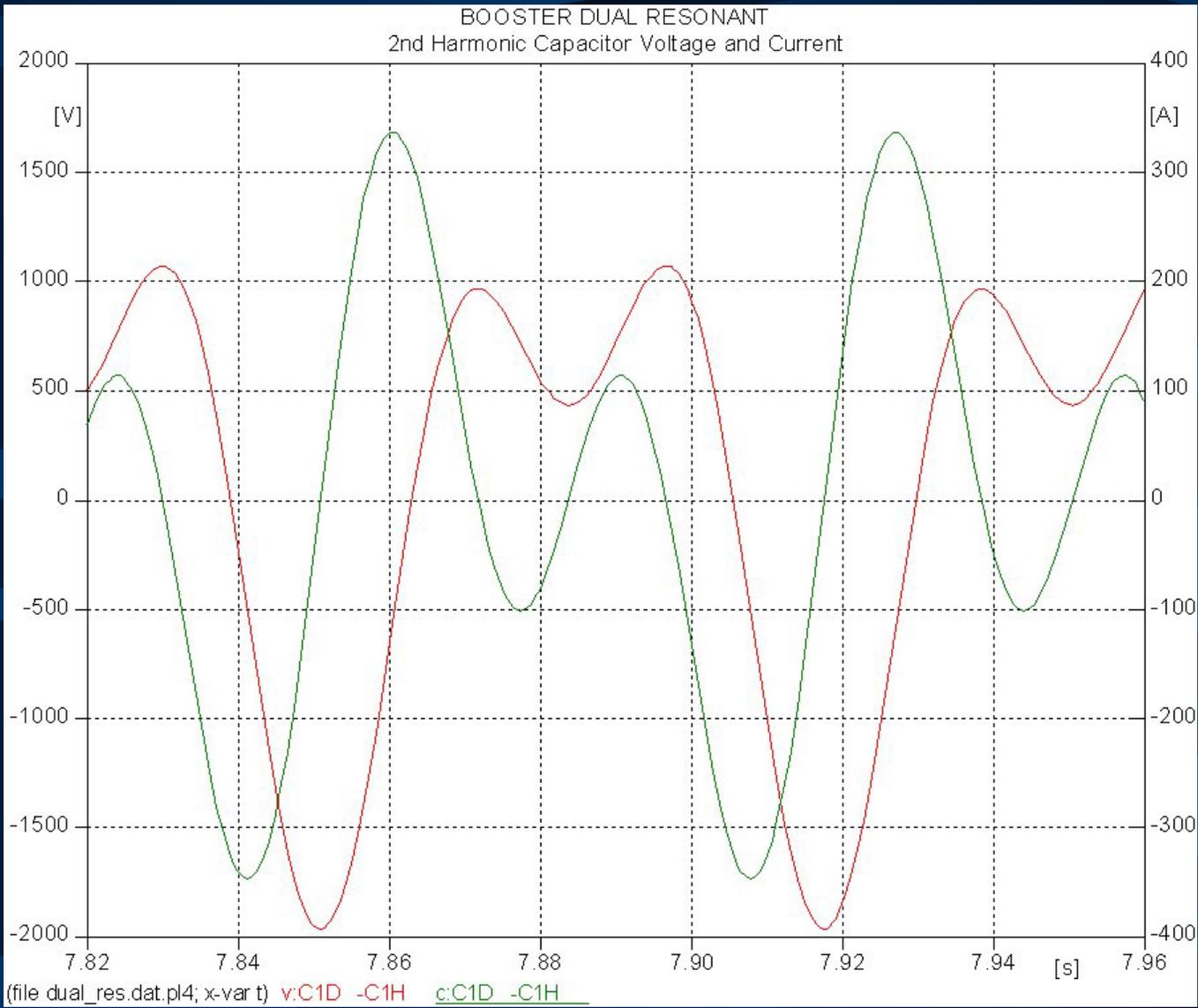
dual_res.dat.pl4: v:C1D -C1G c:C1D -C1G
present.dat.pl4: v:C1D -C1H c:C1D -C1H



2nd Harmonic Capacitor Specifications:

- Capacitance: 1480 uF
- Peak Current: 350 amps
- RMS Current: 200 amps
- Peak Voltage (differential): 2000 volts
- Peak Voltage (common mode): 1500 volts
- Total Losses: < 500 watts

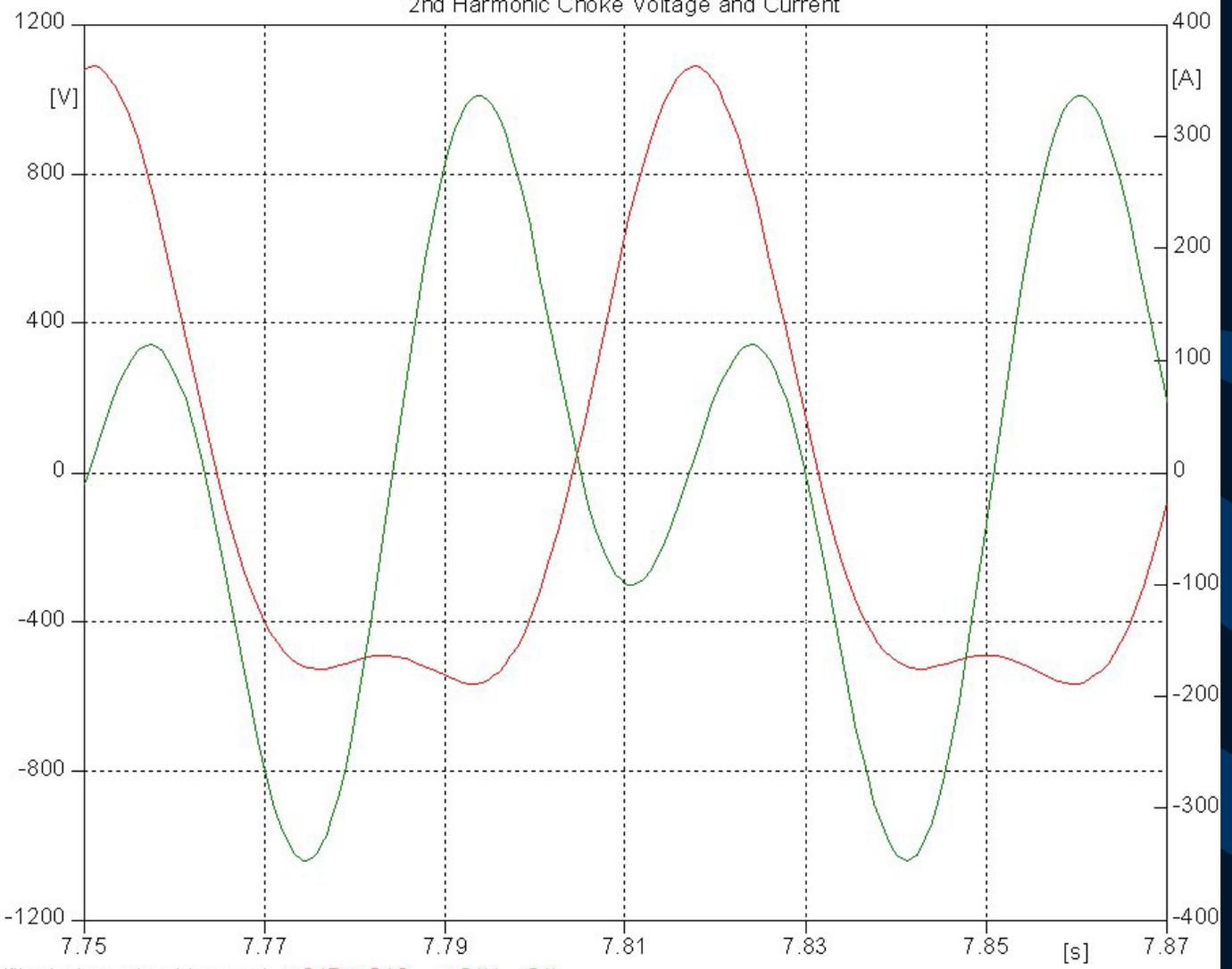BOOSTER DUAL RESONANT
2nd Harmonic Choke Voltage and Current



(file dual_res.dat.pl4; x-var t) v:C1D-v:C1G c:C1H -C1I


2nd Harmonic Choke Specifications:

- Inductance: 26 mH
- Peak Current: 350 amps
- Total RMS Current: 200 amps
- 15 Hz RMS Current: 120 amps
- 30 Hz RMS Current: 155 amps
- Peak Voltage (differential): 1100 volts
- Peak Voltage (common mode): 1500 volts
- DC Resistance (R_{dc}): < 0.010 ohms
- DC Loses ($I^2 * R_{dc}$): 400 watts
- AC Loses (Total loss – DC Loses): < 500 watts


NECESSARY MODIFICATIONS

- Power supplies need to invert
- All power supplies will be needed for normal operation.
- New second harmonic cap bank is needed.
- New second harmonic choke is needed.
- New regulation system needs to be developed.
- Unknown affect on AC line.

REGULATION BLOCK DIAGRAM

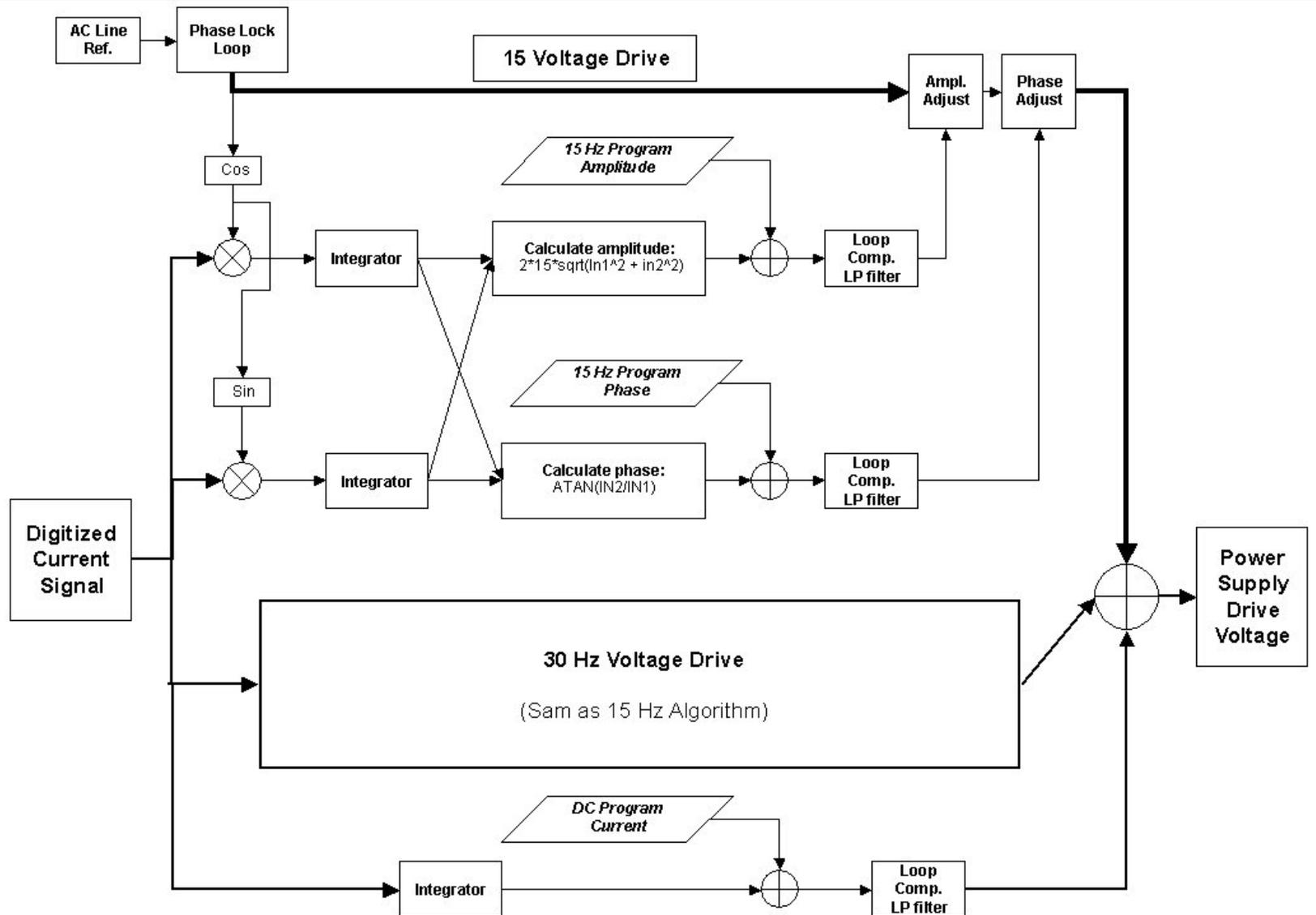

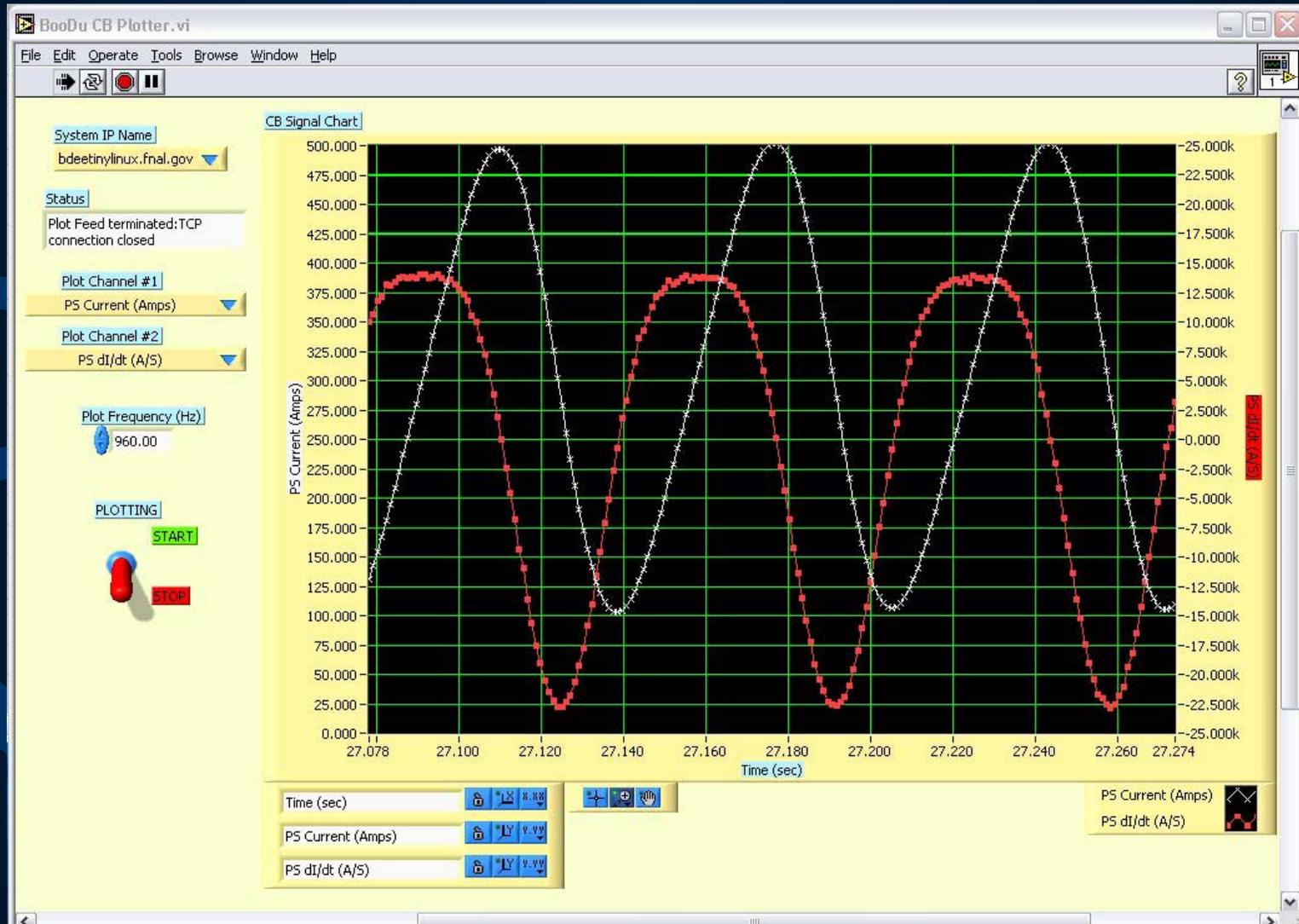Bench-top setup simulating Dual resonant Regulation system using a simple single-card computer




Very crude cost estimate:


- Does not include spares, labor or EDIA.
 - New capacitors: \$4.5k per cell
 $\frac{1}{2} * C * V^2 = 3 \text{ kJoules per cell}$. Assuming \$1.5/joule = \$4.5k per cell. (present caps were \$1/joule)
 - New chokes: \$10k per cell
 $\frac{1}{2} * L * I^2 = 2 \text{ kJoules per cell}$. Assuming \$5.0/joule = \$10k per cell (\$2.5 joule max. for filter choke)
 - largest unknown
 - excessive losses require additional power supply voltage.
 - Unknown costs:
Current regulation, PS inversion, mitigating potential AC line problems, and booster timing changes.
- * Total for 48 cells: about \$700k

Following Slides Compare the
Single Resonant with 18%, 12%, and
9% addition of the 2nd Harmonic

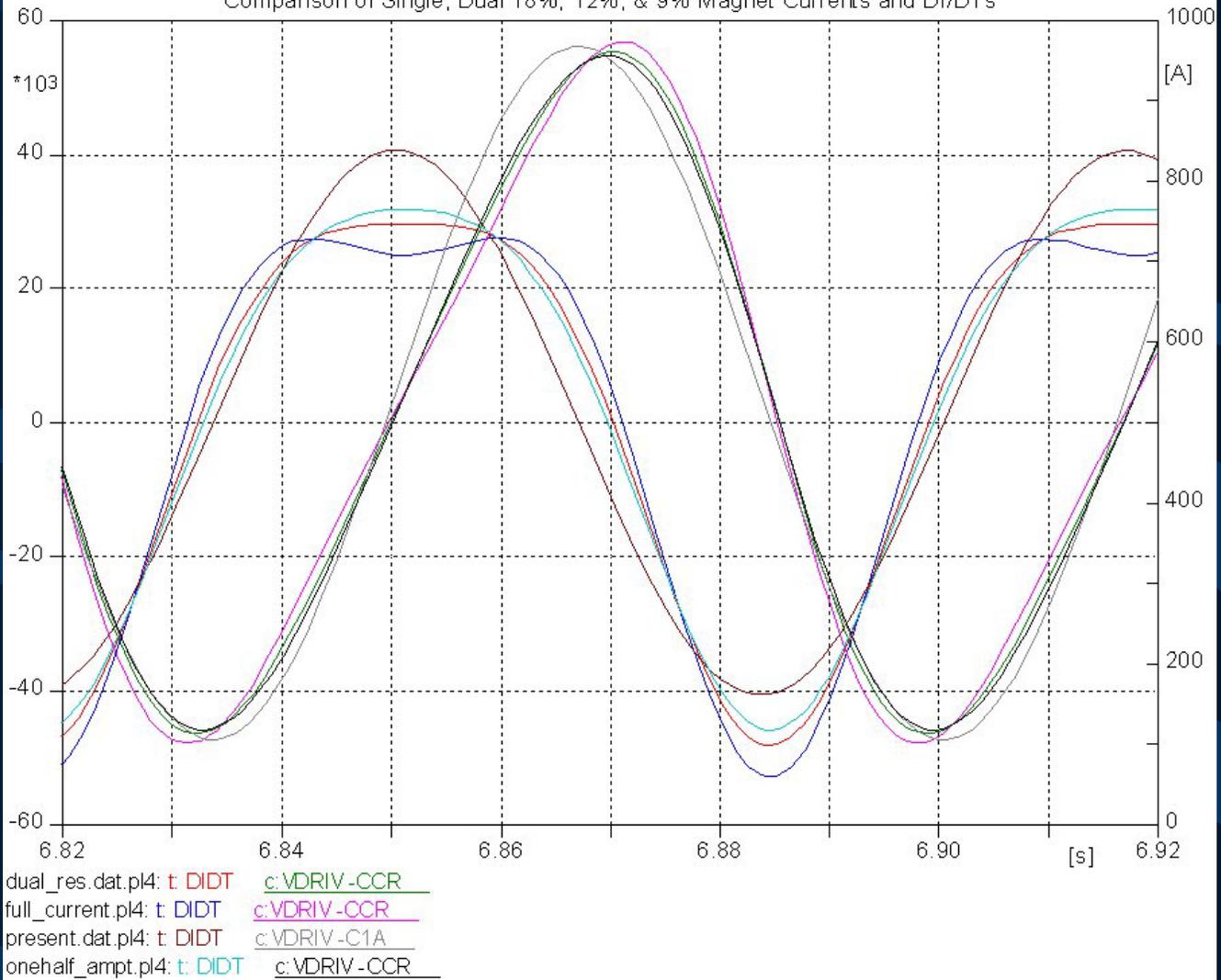BOOSTER DUAL RESONANT
 Comparison of Single, Dual 18%, 12%, & 9% Magnet Currents and DI/DTs




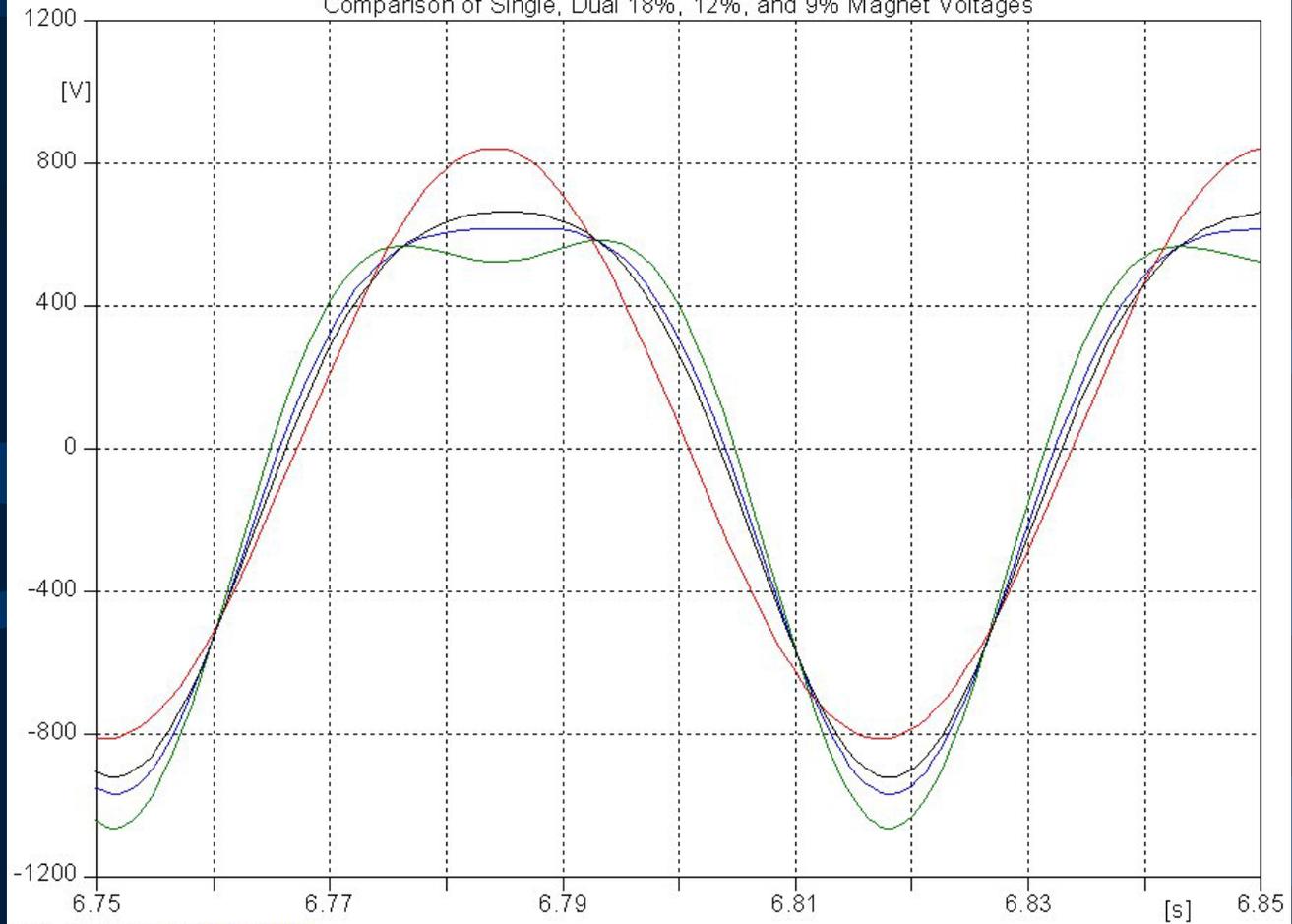BOOSTER DUAL RESONANT
Comparison of Single, Dual 18%, 12%, and 9% Magnet Voltages



dual_res.dat.pl4: v:C1A-v:C1D
full_current.pl4: v:C1A-v:C1D
present.dat.pl4: v:C1A -C1D
onehalf_ampt.pl4: v:C1A-v:C1D

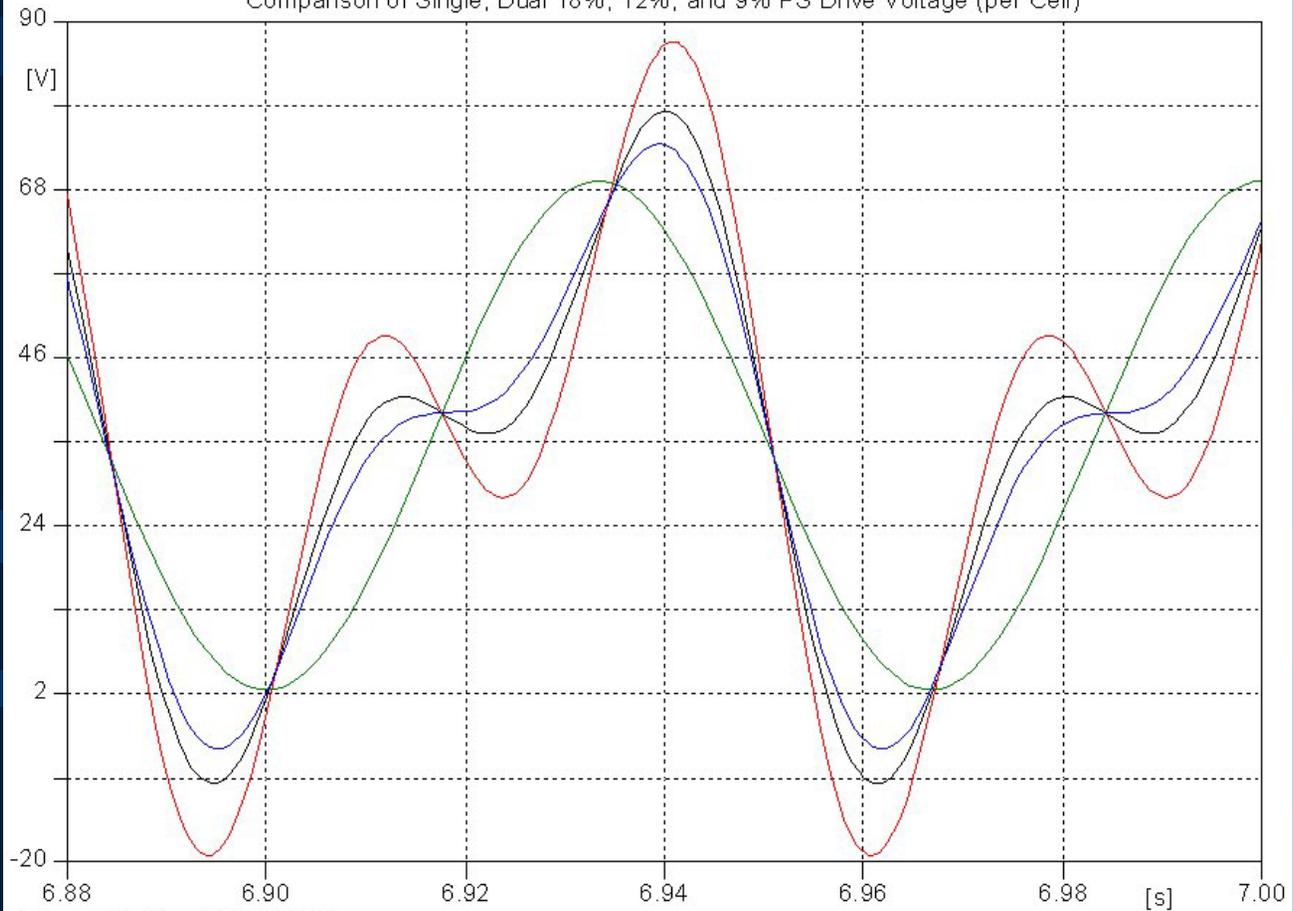
BOOSTER DUAL RESONANT
Comparison of Single, Dual 18%, 12%, and 9% PS Drive Voltage (per Cell)



dual_res.dat.pl4: v:VDRIV -VRET
factors: 0.25
offsets: 0
full_current.pl4: v:VDRIV -VRET
factors: 0.25
offsets: 0
present.dat.pl4: v:VDRIV -VRET
onehalf_ampt.pl4: v:VDRIV -VRET
factors: 0.25
offsets: 0

BOOSTER DUAL RESONANT

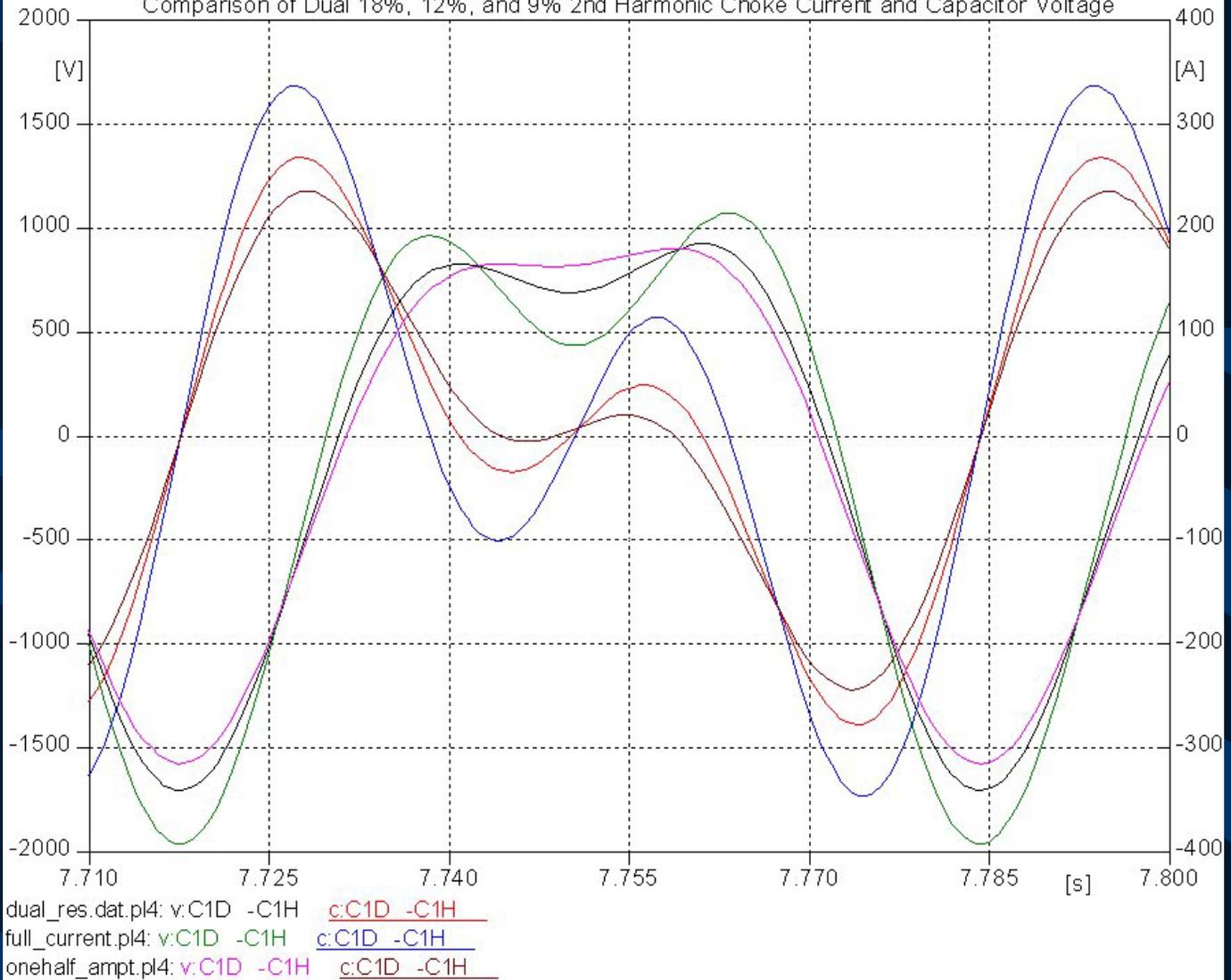Comparison of Dual 18%, 12%, and 9% 2nd Harmonic Choke Current and Capacitor Voltage



DANGER: Disadvantages

- The dual resonance mode will increase the voltage stress on them magnets, inductors, and capacitors by as much as 30%.
- According to the manufacturer, the existing capacitors may be nearing the end of their life.
 - 20 years under operating specs
 - Procured in 1985
 - Life time sensitive to operating voltage and current
- Unknown affect on AC line